

LOGIC.LY 實作


班級:

座號:

姓名:

A	B	\bar{A}	\bar{B}	\bar{A} AND \bar{B}	圖例
0	0	1	1	1	圖一
0	1	1	0	0	圖二
1	0	0	1	0	圖三
1	1	0	0	0	圖四

圖一

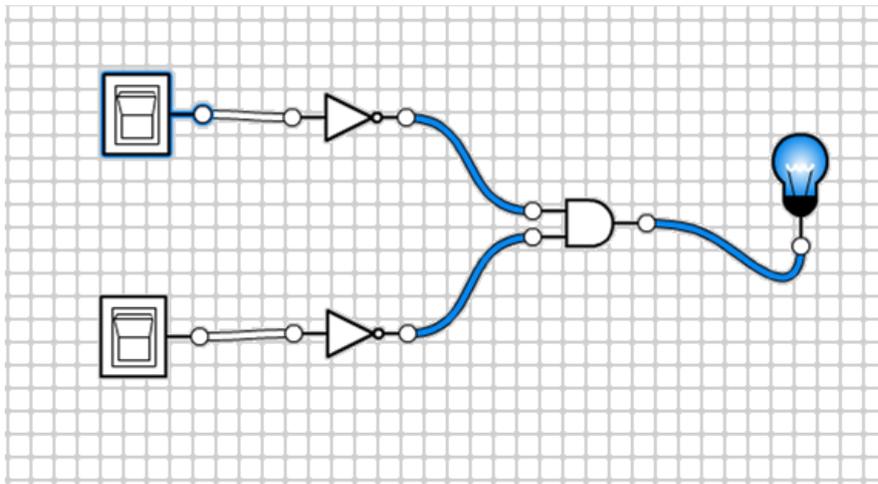

圖二

